

UNIT II

LOGIC GATES



Gates

- ▶ Let's examine the processing of the following six types of gates
 - ▶ NOT
 - ▶ AND
 - ▶ OR
 - ▶ XOR
 - ▶ NAND
 - ▶ NOR
- ▶ Typically, logic diagrams are black and white, and the gates are distinguished only by their shape

NOT Gate

- ▶ A NOT gate accepts one input value and produces one output value

 


Figure 4.1 Various representations of a NOT gate

NOT Gate

- ▶ By definition, if the input value for a NOT gate is 0, the output value is 1, and if the input value is 1, the output is 0
- ▶ A NOT gate is sometimes referred to as an *inverter* because it inverts the input value

AND Gate

- ▶ An AND gate accepts two input signals
- ▶ If the two input values for an AND gate are both 1, the output is 1; otherwise, the output is 0

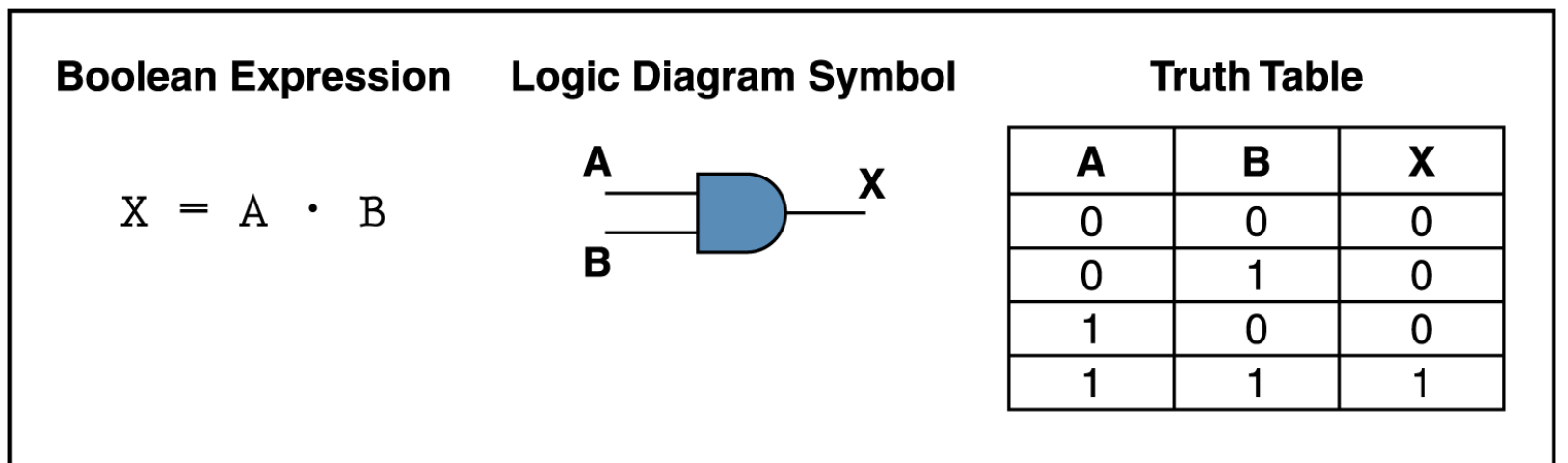


Figure 4.2 Various representations of an AND gate

OR Gate

- ▶ If the two input values are both 0, the output value is 0; otherwise, the output is 1

 


Figure 4.3 Various representations of a OR gate

XOR Gate

- ▶ XOR, or *exclusive* OR, gate
 - ▶ An XOR gate produces 0 if its two inputs are the same, and a 1 otherwise
 - ▶ Note the difference between the XOR gate and the OR gate; they differ only in one input situation
 - ▶ When both input signals are 1, the OR gate produces a 1 and the XOR produces a 0

XOR Gate

 


Figure 4.4 Various representations of an XOR gate

NAND and NOR Gates

- ▶ The NAND and NOR gates are essentially the opposite of the AND and OR gates, respectively

 


Figure 4.5 Various representations of a NAND gate

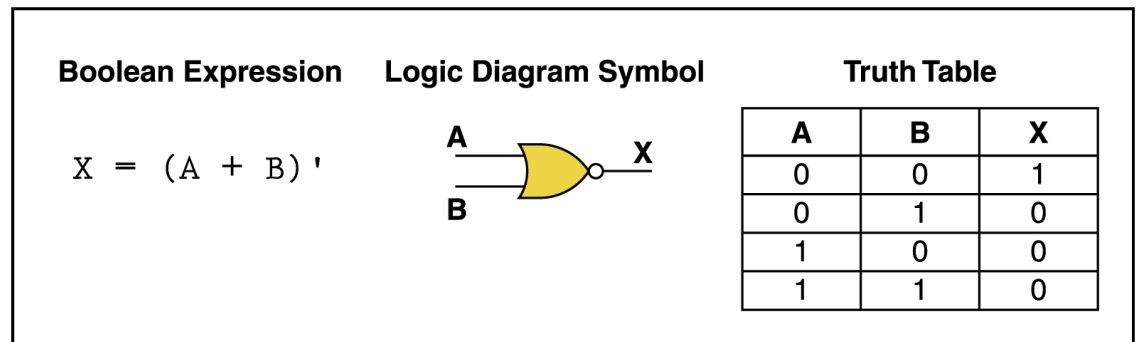


Figure 4.6 Various representations of a NOR gate

Boolean Theorems (Single-Variable)

- $x * 0 = 0$
- $x * 1 = x$
- $x * x = x$
- $x * x' = 0$
- $x + 0 = x$
- $x + 1 = 1$
- $x + x = x$
- $x + x' = 1$

Boolean theorems (multivariable)

- $X Y = Y X$
- $X + (Y + Z) = (X + Y) + Z$
- $X (Y Z) = (X Y) Z$
- $X (Y + Z) = X Y + X Z$
- $(X')' = X$

- We can use Boolean identities to simplify the function:
as follows:

$$\begin{aligned}
 &(X + Y) (X + \bar{Y}) (\overline{XZ}) \\
 &(X + Y) (X + \bar{Y}) (\bar{X} + Z) \\
 &(XX + X\bar{Y} + XY + Y\bar{Y}) (\bar{X} + Z) \\
 &((X + Y\bar{Y}) + X(Y + \bar{Y})) (\bar{X} + Z) \\
 &((X + 0) + X(1)) (\bar{X} + Z) \\
 &X(\bar{X} + Z) \\
 &X\bar{X} + XZ \\
 &0 + XZ \\
 &XZ
 \end{aligned}$$

Idempotent Law (Rewriting)

DeMorgan's Law

Distributive Law

Commutative & Distributive Laws

Inverse Law

Idempotent Law

Distributive Law

Inverse Law

Idempotent Law

Gates with More Inputs

- ▶ Gates can be designed to accept three or more input values
- ▶ A three-input AND gate, for example, produces an output of 1 only if all input values are 1

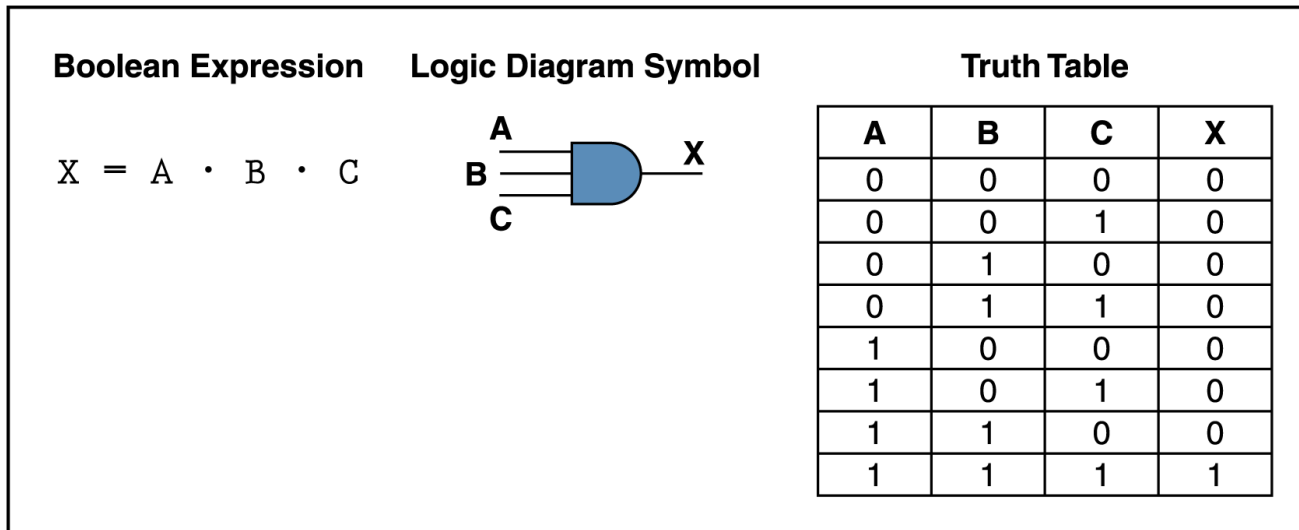


Figure 4.7 Various representations of a three-input AND gate

Prove the following identities using truth table

Perfect Induction Method

$$(X + Y) (X + Z) = X + YZ$$

X	Y	Z	X+Y	X+Z	YZ	(X+Y)(X+Z)	X+YZ
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1
1	0	1	1	1	0	1	1
1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	1

$$\text{R.H.S.} = \text{L.H.S.}$$

$$X + \overline{X} Y = X + Y$$

X	Y	\overline{X}	$\overline{X} Y$	$X + \overline{X} Y$	$X + Y$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

L.H.S. = R.H.S.

$$X \cdot (\overline{X} + Y) = X \cdot Y$$


De Morgan's Theorems:

$$(i) \overline{X + Y} = \overline{X} \cdot \overline{Y}$$

$$(ii) \overline{X \cdot Y} = \overline{X} + \overline{Y}$$

Combinational Circuits

 - ▶ Gates are combined into circuits by using the output of one gate as the input




Combinational Circuits

A	B	C	D	E	X
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

- ▶ Because there are three inputs to this circuit, eight rows are required to describe all possible input combinations
- ▶ This same circuit using Boolean algebra:
 $(AB + AC)$

Now let's go the other way; let's take a Boolean expression and draw

 
- Consider the following Boolean expression: $A(B + C)$




A	B	C	$B + C$	$A(B + C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

- Now compare the final result column in this truth table to the truth table for the previous example
 - They are identical


NAND as NOT

 


NAND as OR

 


NAND as AND

 


NOR as OR

 

NOR as AND

 


NOR as NOT

 

Realization of Logic Gates Using Universal Gates


$$F = AB + CD + E$$

Logic representation of F:

 


$$F = AB + CD + E$$

NAND implementation

 

NOR implementation

 

Standard Forms of Boolean Expressions

- All Boolean expressions, regardless of their form, can be converted into either of two standard forms:
 - The sum-of-products (SOP) form
 - The product-of-sums (POS) form

Sum-of-Products (SOP)

Canonical Forms-Minterms and Maxterms

x	y	z	minterm	designati on	maxterm	designati on
0	0	0	$\overline{x} \overline{y} \overline{z}$	m_0	$x+y+z$	M_0
0	0	1	$\overline{x} \overline{y} z$	m_1	$x+y+\overline{z}$	M_1
0	1	0	$\overline{x} y \overline{z}$	m_2	$x+\overline{y}+z$	M_2
0	1	1	$\overline{x} y z$	m_3	$x+\overline{y}+\overline{z}$	M_3
1	0	0	$x \overline{y} \overline{z}$	m_4	$\overline{x}+y+z$	M_4
1	0	1	$x \overline{y} z$	m_5	$\overline{x}+y+\overline{z}$	M_5
1	1	0	$x y \overline{z}$	m_6	$\overline{x}+\overline{y}+z$	M_6
1	1	1	$x y z$	m_7	$\overline{x}+\overline{y}+\overline{z}$	M_7

(AND terms)

(OR terms)

The Sum-of-Products (SOP) Form

- An SOP expression
→ when two or more product terms are summed by Boolean addition.

– Examples:

$$AB + ABC$$

$$ABC + CDE + \overline{BCD}$$

$$\overline{AB} + \overline{ABC} + AC$$


– Also:

$$A + \overline{ABC} + \overline{BCD}$$


Implementation of an SOP

$$X = AB + BCD + AC$$

- **AND/OR implementation**

 

- **NAND/NAND implementation**

 

Product-of-Sums (POS)

The Product-of-Sums (POS) Form

- When two or more sum terms are multiplied, the result expression is a product-of-sums (POS):

- Examples:

$$(\bar{A} + B)(A + \bar{B} + C)$$

$$(\bar{A} + \bar{B} + \bar{C})(C + \bar{D} + E)(\bar{B} + C + D)$$


$$(A + B)(A + \bar{B} + C)(\bar{A} + C)$$

- Also: $\bar{A}(\bar{A} + \bar{B} + C)(B + C + \bar{D})$

Implementation of a POS

$$X = (A + B)(B + C + D)(A + C)$$

- **OR/AND implementation**

 

The Standard POS Form

- A standard POS expression is one in which *all* the variables in the domain appear in each sum term in the expression.
 - Example $(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + \bar{B} + C + D)(A + B + \bar{C} + D)$
- Standard POS expressions are important in:
 - Constructing truth tables
 - The Karnaugh map simplification method

Converting SOP Expressions to Truth Table Format (example)

- Develop a truth table for the standard SOP expression

$$\overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$$

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\overline{A}\overline{B}C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A\overline{B}\overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Converting POS Expressions to Truth Table Format (example)

- Develop a truth table for the standard SOP expression

$$(A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})$$

$$(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \bar{B} + C)$
0	1	1	0	$(A + \bar{B} + \bar{C})$
1	0	0	1	
1	0	1	0	$(\bar{A} + B + \bar{C})$
1	1	0	0	$(\bar{A} + \bar{B} + C)$
1	1	1	1	

The Karnaugh Map

The 2 Variable K-Map

A. SOP: -

	B	\bar{B}	B
A	0	1	
\bar{A}	0	$\bar{A}.\bar{B}$	$\bar{A}.B$
A	1	$A.\bar{B}$	$A.B$

B. POS: -

	B	B	\bar{B}
A	0	1	
A	0	$A+B$	$A+\bar{B}$
\bar{A}	1	$\bar{A}+B$	$\bar{A}+\bar{B}$

The 3 Variable K-Map

- There are 8 cells as shown:

		C	
		0	1
AB	00	$\overline{A}\overline{B}\overline{C}$	$\overline{A}\overline{B}C$
	01	$\overline{A}B\overline{C}$	$\overline{A}BC$
11	$AB\overline{C}$	ABC	
10	$A\overline{B}\overline{C}$	$A\overline{B}C$	

The 4-Variable K-Map

		CD			
		00	01	11	10
AB	00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}CD$	$\bar{A}\bar{B}C\bar{D}$
	01	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BCD$	$\bar{A}BC\bar{D}$
	11	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABCD$	$ABC\bar{D}$
	10	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B}CD$	$A\bar{B}C\bar{D}$

Mapping a Nonstandard SOP Expression

- Map the following SOP expressions on K-maps:

$$\bar{A} + A\bar{B} + ABC\bar{C}$$

$$\bar{B}\bar{C} + A\bar{B} + ABC\bar{C} + A\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}CD$$

K-Map Simplification of SOP Expressions

- After an SOP expression has been mapped, we can do the process of *minimization*:
 - Grouping the 1s
 - Determining the minimum SOP expression from the map

Grouping the 1s (rules)

- 1. A group must contain either 1,2,4,8,or 16 cells (depending on number of variables in the expression)**
- 2. Each cell in a group must be adjacent to one or more cells in that same group, but all cells in the group do not have to be adjacent to each other.**
- 3. Always include the largest possible number of 1s in a group in accordance with rule 1.**
- 4. Each 1 on the map must be included in at least one group. The 1s already in a group can be included in another group as long as the overlapping groups include noncommon 1s.**

Grouping the 1s (example)

AB \ C	0	1
00	1	
01		1
11	1	1
10		

AB \ C	0	1
00	1	1
01	1	
11		1
10	1	1


Grouping the 1s (example)

		CD			
		00	01	11	10
AB	00	1	1		
	01	1	1	1	1
	11				
	10		1	1	

		CD			
		00	01	11	10
AB	00	1			1
	01	1	1		1
	11	1	1		1
	10	1		1	1

Determining the Minimum SOP Expression from the Map (example)

$$B + \bar{A}C + A\bar{C}D$$

 

Determining the Minimum SOP Expression from the Map (exercises)


		C	
		0	1
AB	00	1	
	01		1
	11	1	1
	10		

$$AB + BC + \overline{A}\overline{B}\overline{C}$$


		C	
		0	1
AB	00	1	1
	01	1	
	11		1
	10	1	1

$$\overline{B} + \overline{A}\overline{C} + AC$$

 Determining the Minimum SOP Expression from the Map (exercises)



 
$$\bar{A}B + \bar{A}\bar{C} + A\bar{B}D$$



$$\bar{D} + \bar{A}\bar{B}C + BC$$

 Determining the Minimum SOP Expression from the Map (example)



$$B + \bar{A}C + A\bar{C}D$$

Determining the Minimum SOP Expression from the Map (exercises)


		C	
		0	1
AB	00	1	
	01		1
	11	1	1
	10		

$$AB + BC + \overline{A}\overline{B}\overline{C}$$


		C	
		0	1
AB	00	1	1
	01	1	
	11		1
	10	1	1

$$\overline{B} + \overline{A}\overline{C} + AC$$

 Determining the Minimum SOP Expression from the Map (exercises)


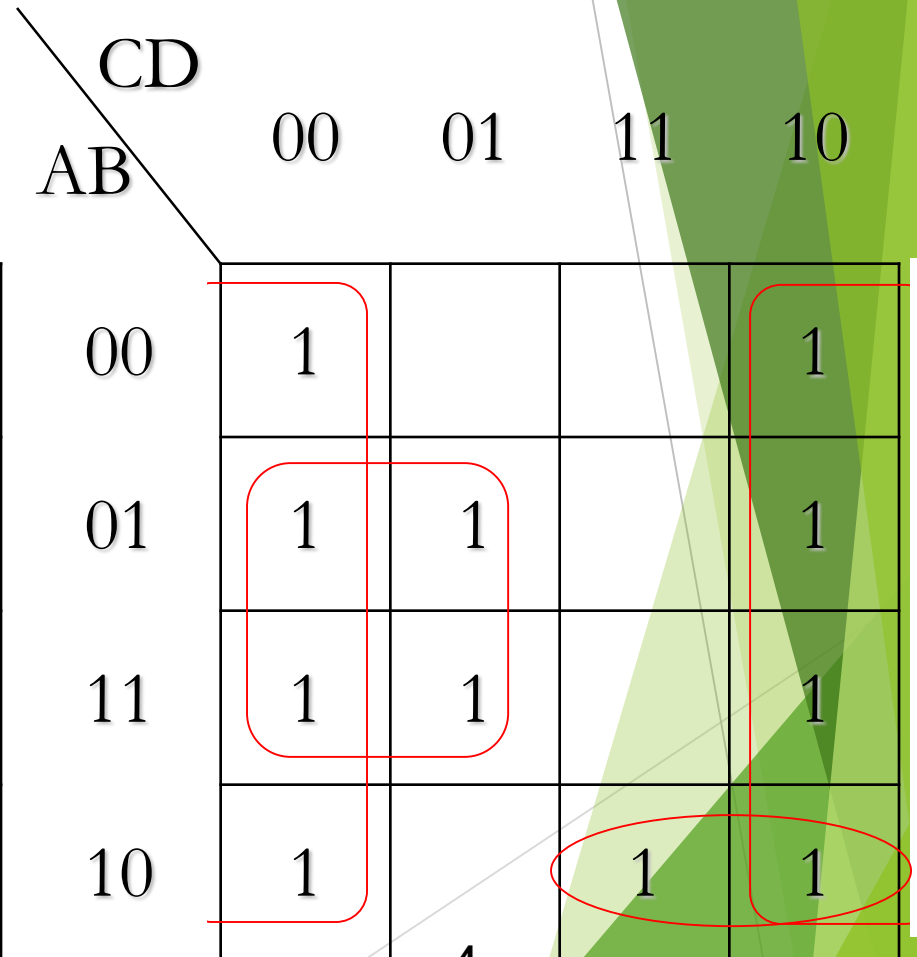
$$\bar{A}B + \bar{A}\bar{C} + A\bar{B}D$$



$$\bar{D} + \bar{A}\bar{B}C + BC$$

Practicing K-Map (SOP)

$$\overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + A\overline{B}\overline{C}$$

$$\overline{B} + \overline{A}C$$

$$\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + A\overline{B}C\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D}$$

$$\overline{D} + \overline{B}C$$

Mapping Directly from a Truth Table

I/P			O/P
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

		C	
		0	1
AB	00	1	
	01		
	11	1	1
	10	1	

“Don’t Care” Conditions

- Sometimes a situation arises in which some input variable combinations are not allowed, i.e. BCD code:
 - There are six invalid combinations: 1010, 1011, 1100, 1101, 1110, and 1111.
- Since these unallowed states will never occur in an application involving the BCD code → they can be treated as “don’t care” terms with respect to their effect on the output.
- The “don’t care” terms can be used to advantage on the K-map.

“Don’t Care” Conditions

INPUTS				O/P
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

	CD			
	00	01	11	10
AB	00			
	01		1	
	11	x	x	x
	10	1	1	x
				x

Without “don’t care”
 $Y = ABC + ABCD$

With “don’t care”
 $Y = A + BCD$

K-Map POS Minimization

- **The approaches are much the same (as SOP) except that with POS expression, 0s representing the standard sum terms are placed on the K-map instead of 1s.**

Mapping a Standard POS Expression (full example)

The expression:


$$(A+B+C)(A+\bar{B}+C)(\bar{A}+\bar{B}+C)(\bar{A}+B+\bar{C})$$



		C	
		0	1
AB	00	0	
	01	0	
	11	0	
	10		0

K-map Simplification of POS Expression
 
$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)$$



Shorthand: \sum and \prod

- $f_1(a,b,c) = \sum m(1,2,4,6)$, where \sum indicates that this is a sum-of-products form, and $m(1,2,4,6)$ indicates that the minterms to be included are m_1 , m_2 , m_4 , and m_6 .
- $f_1(a,b,c) = \prod M(0,3,5,7)$, where \prod indicates that this is a product-of-sums form, and $M(0,3,5,7)$ indicates that the maxterms to be included are M_0 , M_3 , M_5 , and M_7 .
- Since $m_j = M_j'$ for any j ,
 $\sum m(1,2,4,6) = \prod M(0,3,5,7) = f_1(a,b,c)$

Conversion Between Canonical Forms

- Replace \sum with \prod (or *vice versa*) and replace those j 's that appeared in the original form with those that do not.

- Example:

$$\begin{aligned}f_1(a,b,c) &= a'b'c + a'bc' + ab'c' + abc' \\ &= m_1 + m_2 + m_4 + m_6 \\ &= \sum(1,2,4,6) \\ &= \prod(0,3,5,7) \\ &= (a+b+c) \cdot (a+b'+c') \cdot (a'+b+c') \cdot (a'+b'+c')\end{aligned}$$

More Examples

- $f_1(x, y, z) = \sum m(2,3,5,7)$

- $f_1(x, y, z) = x'y + xz$

x \ yz	00	01	11	10
0			1	1
1		1	1	

- $f_2(x, y, z) = \sum m(0,1,2,3,6)$

- $f_2(x, y, z) = x' + yz'$

1	1	1	1
			1

Example

- Simplify the following Boolean function $(A,B,C,D) = \sum m(0,1,2,4,5,7,8,9,10,12,13)$.
- First put the function $g()$ into the map, and then group as many 1s as possible.

cd

ab


1	1		1
1	1	1	
1	1		
1	1		1

1	1		1
1	1	1	
1	1		
1	1		1

$$g(A,B,C,D) = c' + b'd' + a'bd$$


Implement the circuit for the for given minterm(SOP) function (NAND)

► $F = ABC + A'BC + ABC'$

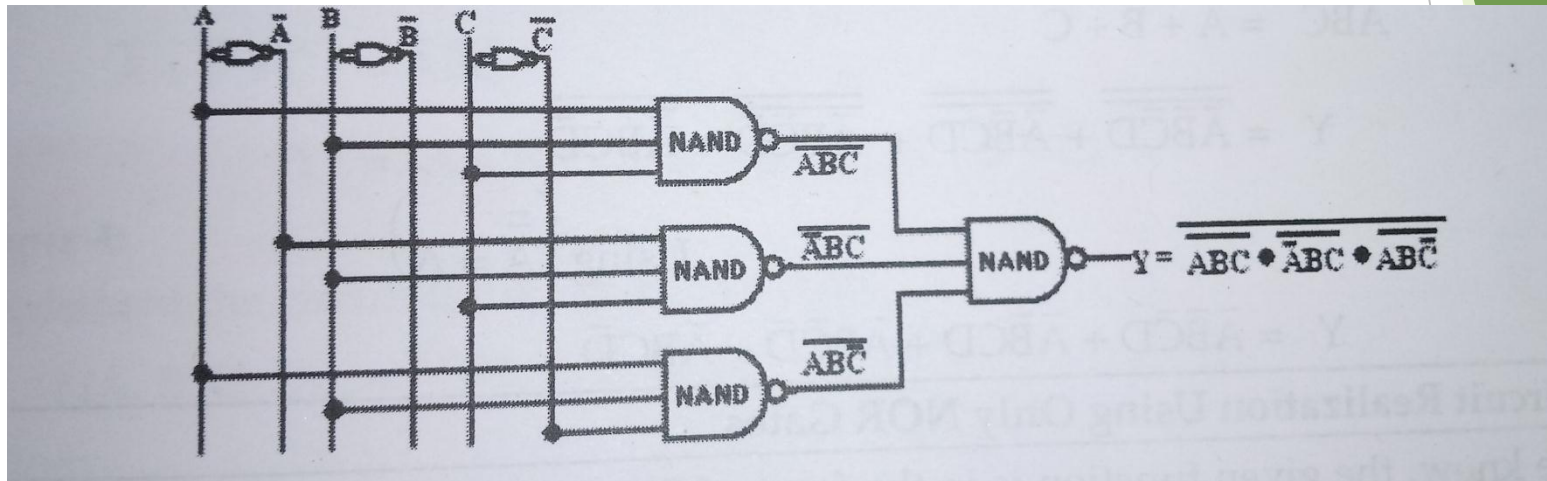


Implement the circuit for the given function

► $f(A,B,C,D) = \sum m(1,3,4,6)$

 

Implement the circuit for the given function

► $f(A,B,C) = (A+B+C)(A'+B+C)(A+B+C')$

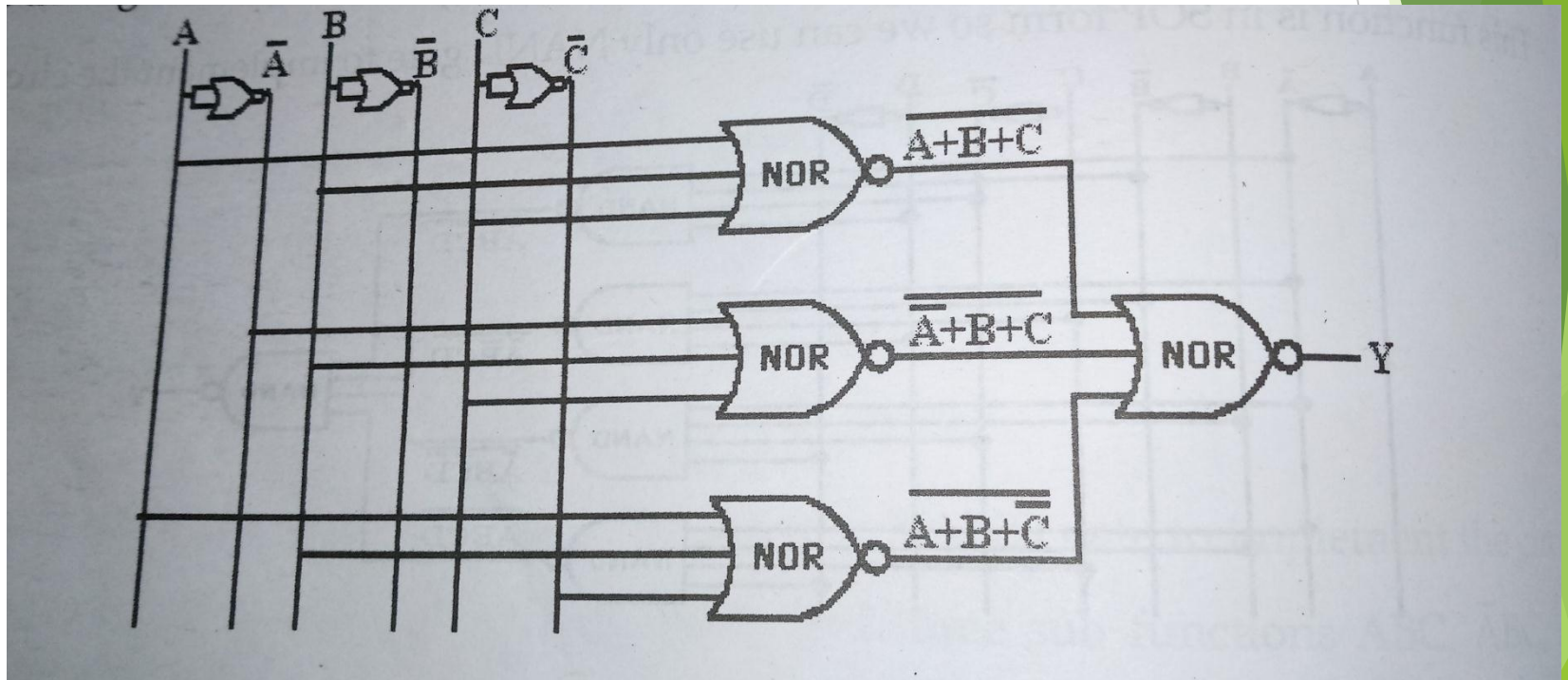

Implement the circuit for the given function

